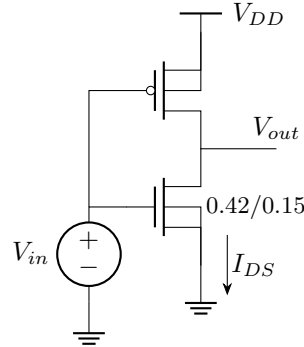


EE5311 Digital IC Design: Assignment 2
Inverter - DC characteristics

$$V_{Tn} = 0.7 \text{ V}, \quad \mu_n = 0.025 \text{ m}^2/\text{V} \cdot \text{s}, \quad C_{oxn} = 8.34 \text{ fF}/\mu\text{m}^2, \quad v_{satn} = 8 \times 10^4 \text{ m/s}, \quad \lambda_n = 0.2/\text{V}$$


$$|V_{Tp}| = 0.7 \text{ V}, \quad \mu_p = 0.009 \text{ m}^2/\text{V} \cdot \text{s}, \quad C_{oxp} = 8.16 \text{ fF}/\mu\text{m}^2, \quad v_{satp} = 3 \times 10^4 \text{ m/s}, \quad \lambda_p = 0.2/\text{V}$$

1. For the static inverter shown below



find $(W/L)_p$ so that the inverter threshold voltage $V_{th} = V_{DD}/2$. Plot the DC transfer characteristic.

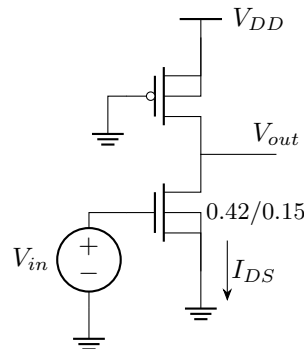- (a) Plot the derivative and obtain the noise margins.
 - (b) How does the characteristic change if $(W/L)_p$ is increased by a factor of 10? Decreased by a factor of 10?
 - (c) Obtain the DC transfer characteristic for V_{DD} ranging from 0.2V to 1.8V in steps of 0.2V. Plot the I_{DS} vs V_{in} for all these supply voltages. Can it be used as an inverter for these supply voltages? If the circuit does not behave as an inverter for some supply voltage, what change can be made to the pMOS width or length to turn it into an inverter?
 - (d) For $V_{DD} = 0.8, 1.8\text{V}$, find the peak I_{DS} and compare it with the analytical value.
2. Consider the pseudo-nMOS inverter shown below.



Size the pMOS transistor so that $V_{OL} = 0.1\text{V}$. Using Ngspice, plot the DC transfer characteristic.

- (a) Find the inverter threshold voltage.
- (b) Plot the derivative and obtain the high and low noise margins. Do an approximate calculation using the analytical models and compare with the simulated value.
- (c) Assuming $V_{in} = V_{DD}$, find the average power dissipated and compare with the analytically obtained value.