

DIC Tutorial 2 Report

Ishan Aji Hassan - EE23B097

August 16, 2026

Question 1

Part (a)

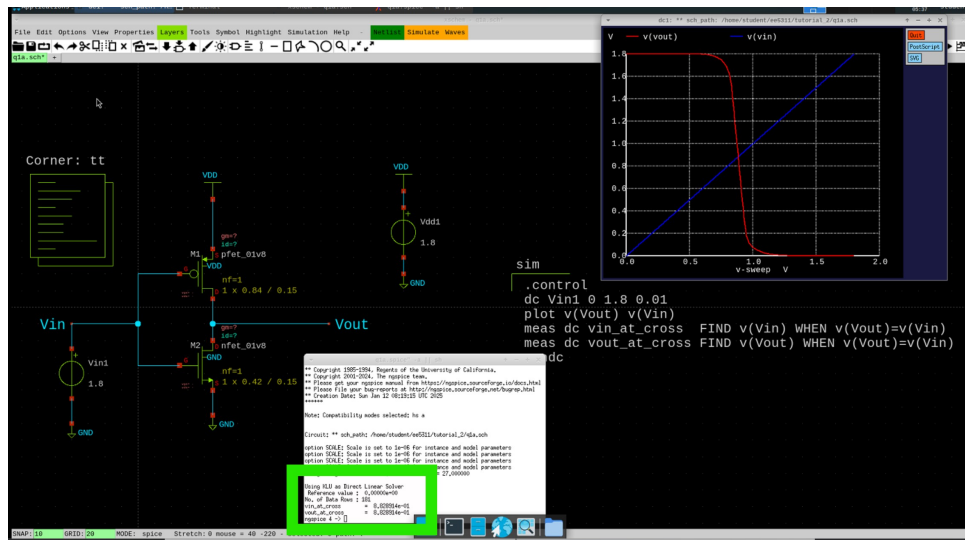


Figure 1: Voltage Transfer Characteristic (VTC) for Question 1a.

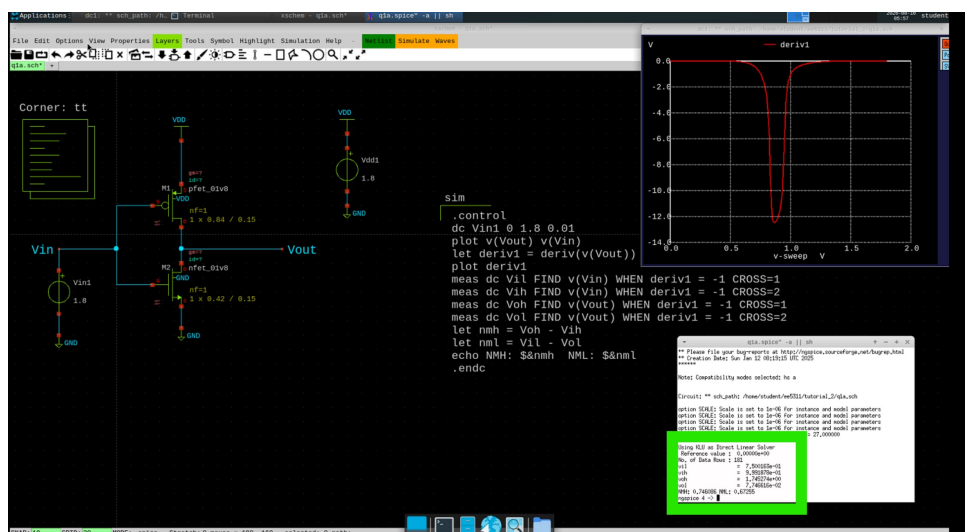


Figure 2: Derivative plot and noise margin measurements for Question 1a.

Part (b)

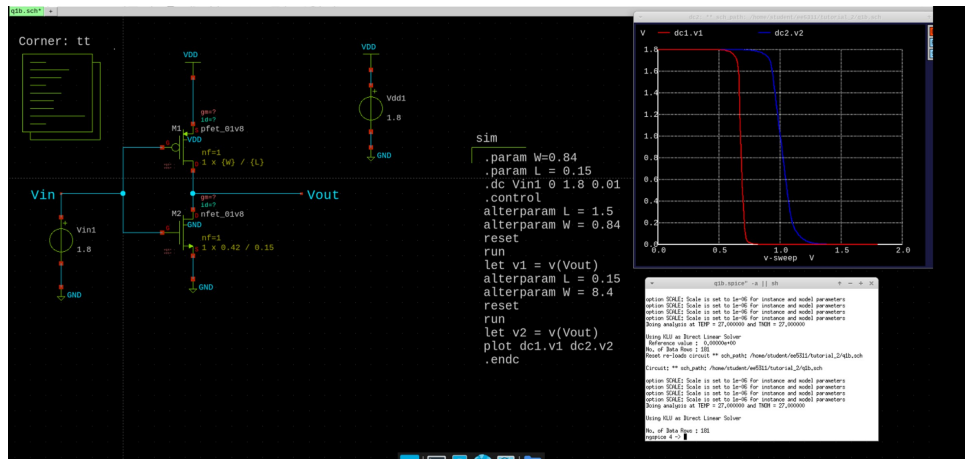


Figure 3: Parametric sweep results for Question 1b.

Part (c)

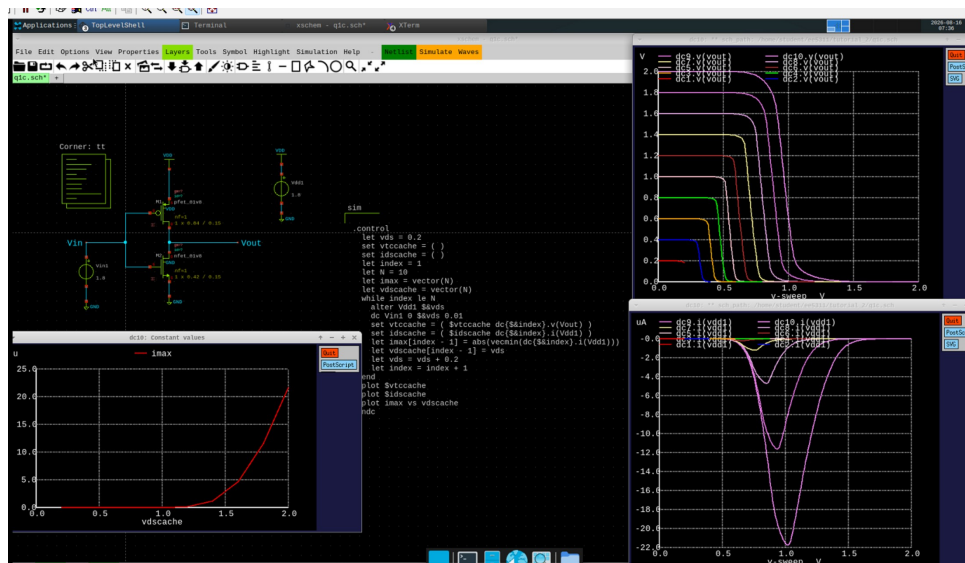


Figure 4: Nested DC sweep and maximum current tracking for Question 1c.

Question 2

Part (a)

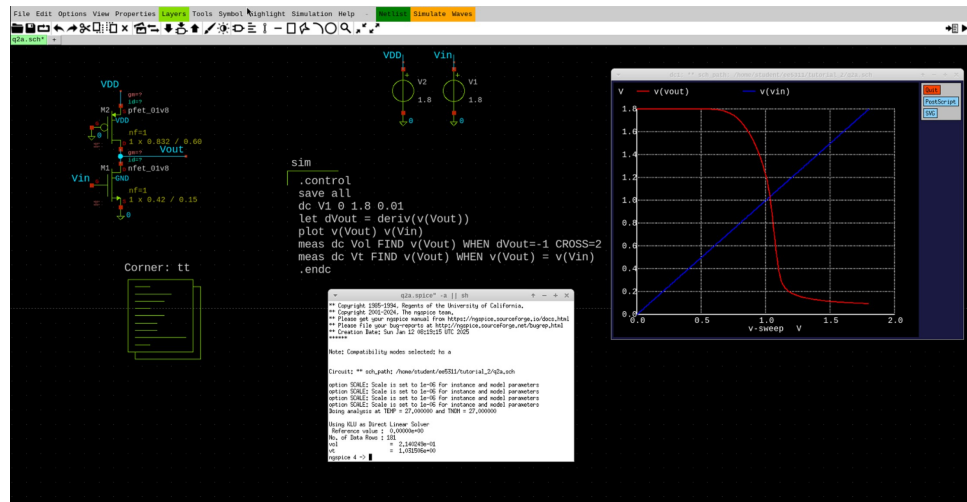


Figure 5: Pseudo-NMOS inverter transfer characteristics for Question 2a.

Part (b)

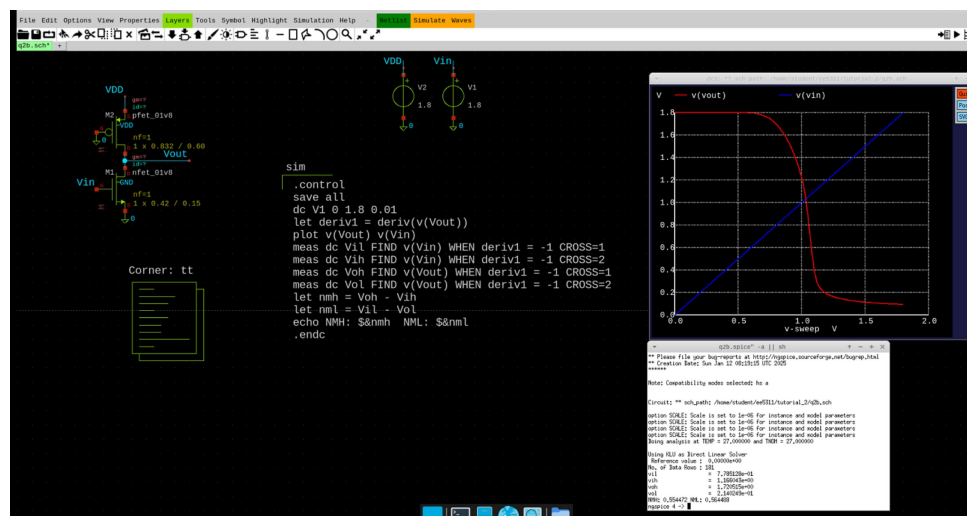


Figure 6: Noise margin extraction using the derivative method for Question 2b.

Part (c)

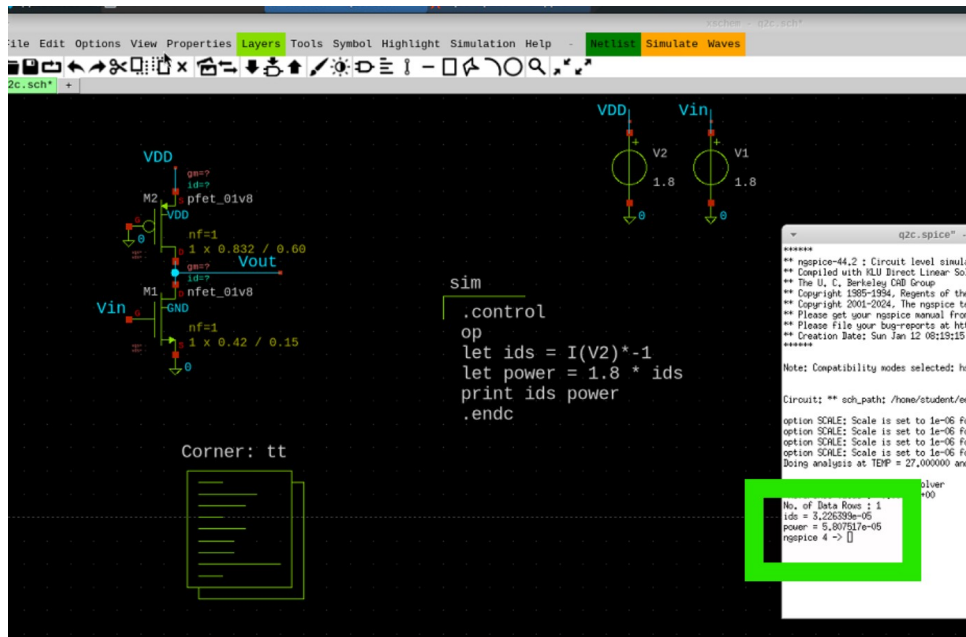


Figure 7: Operating point analysis and static power calculation for Question 2c.